


3.2 中 HfO_2 的相对介电常数在不同的排列下不一样，所以只要式子对即可

3.2 The answer to this question is based on the difference in dielectric constant between SiO_2 ($k=3.9$) and HfO_2 ($k=20$). The oxide thickness would be $2 \text{ nm} \cdot (20/3.9) = 10.26 \text{ nm}$.

3.6 Metal1 has a 2×2 contact with an overlap of 1 on each side, requiring a 4λ width. The metal spacing is 3λ , so the pitch is 7λ if contacts can meet head to head.

A denser wiring strategy is to offset contacts. The pitch is reduced by half the distance that the contact extends beyond minimum metal width, thus giving a 6.5λ pitch.

 4.2 The rising delay is $(R/2) \cdot 2C + R \cdot (5C + 5hC) = (6 + 5h)RC$ and the falling delay is $R \cdot 2C + R \cdot (5C + 5hC) = (7 + 5h)RC$.



4.4

① 下降最坏情况，P管网络最上方1个不导通

$$t_{pdf} = (nC + 2nC) \cdot R + 2nC \cdot R \cdot (n-1)$$

$$= (2n^2 + n)RC$$

② 上升最坏情况

$$t_{pdr} = (nC + 2nC) \cdot R + \sum_{i=1}^{n-1} 2nC \cdot \frac{iR}{n}$$

$$= (n^2 + 2n)RC$$

当 $n \geq 1$, 恒有 $(2n^2 + n) > (n^2 + 2n)$

综上，最坏情况下寄生延时为 $(2n^2 + n)RC$

- 4.10 (a) should be faster than (b) because the NAND has the same parasitic delay but lower logical effort than the NOR. In each design, $H = 6$, $B = 1$, $P = 1 + 2 = 3$. For (a), $G = (4/3) * 1 = (4/3)$. $F = GBH = 8$. $f = 8^{1/2} = 2.8$. $D = 2f + P = 8.6 \tau$. $x = 6C * 1 / f = 2.14C$. For (b), $G = 1 * (5/3)$. $F = GBH = 10$. $f = 10^{1/2} = 3.2$. $D = 2f + P = 9.3 \tau$. $x = 6C * (5/3) / f = 3.16C$.
- 4.20 NAND: $g = (\mu + k) / (\mu + 1)$; NOR: $g = (\mu k + 1) / (\mu + 1)$. As μ increases, NOR gates get worse compared to NAND gates because the series pMOS devices become more expensive.