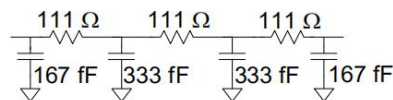


5.2 Dynamic power consumption will go down because it is quadratically dependent on V_{DD} . Static power will go up because subthreshold leakage is exponentially dependent on V_t .

5.4 The signal makes 4 transitions in 10 cycles, so the activity factor is $(1/2)(4/10) = 0.2$.

5.10 For a 2% delay increase, the supply should droop by less than about 2% of V_{DD} (e.g. 20 mV @ 1.0 V). Thus the effective resistance must be $R = 20 \text{ mV} / 100 \text{ mA} = 0.2 \Omega$. This requires a width of $W = 2.5 \text{ k}\Omega \cdot \mu\text{m} / 0.2 \Omega = 12.5 \text{ mm}$.

6.2 The wire width is $1.2 \mu\text{m}$ so the wire is $5000 \mu\text{m} / 1.2 \mu\text{m} = 4167$ squares in length. The total resistance is $(0.08 \Omega/\text{sq}) \cdot (4167 \text{ sq}) = 333 \Omega$. The total capacitance is $(0.2 \text{ fF}/\mu\text{m}) \cdot (5000 \mu\text{m}) = 1 \text{ pF}$.



6.8

地址: 中国 安徽 合肥市金寨路96号 邮编: 230026
电话: 0551-63602184 传真: 0551-63631760 Http://www.ustc.edu.cn

6.8. 令中间一级的尺寸为 W , 有 $R_i = R_0/W$, $C_i = W C_{in0} + W C_{pi0}$

$$t_{pd} = R_{i-1} \cdot C_{pi,i-1} + (R_{i-1} + R_{wi,i-1}) C_{wi,i-1} + (R_{i-1} + R_{wi,i-1}) \cdot W C_{in0} + (R_{i-1} + R_{wi,i-1} + \frac{R_0}{W}) W C_{pi0}$$

$$+ (R_{i-1} + R_{wi,i-1} + \frac{R_0}{W} + R_{wi}) C_{wi} + (\dots + \frac{R_0}{W} + \dots) C_{in,i+1} + (\dots + \frac{R_0}{W} + \dots) C_{pi,i+1}$$

$$\frac{\partial t_{pd}}{\partial W} = (R_{i-1} + R_{wi,i-1}) C_{in0} + (R_{i-1} + R_{wi,i-1}) C_{pi0} - \frac{R_0 C_{wi}}{W^2} - \frac{R_0 C_{in,i+1}}{W^2} - \frac{R_0 C_{pi,i+1}}{W^2} = 0$$

$$\therefore (R_{i-1} + R_{wi,i-1}) (C_{in0} + C_{pi0}) \cdot W = \frac{R_0}{W} \cdot (C_{wi} + C_{in,i+1} + C_{pi,i+1})$$

$$\therefore (R_{i-1} + R_{wi,i-1}) C_i = R_i (C_{wi} + C_{i+1})$$

由(6.26)式:

$$t_{pd} = \frac{R}{W} [C_w L + N C W (1 + P_{inv})] + R_w \left(\frac{C_w L}{2N} + C W \right) \quad (6.27)$$

$$\frac{\partial t_{pd}}{\partial N} = C R (1 + P_{inv}) - \frac{R_w C_w L^2}{2N^2}$$

$$\frac{\partial t_{pd}}{\partial N} = 0 \Rightarrow \frac{L}{N} = \sqrt{\frac{2RC(1+P_{inv})}{R_w C_w}} \quad (6.27)$$

$$\text{代入 } P_{inv} = 0.5, \frac{L}{N} = \sqrt{\frac{3RC}{R_w C_w}} = 0.77 \sqrt{\frac{5RC}{R_w C_w}} = 0.77 \sqrt{\frac{FQ_d}{R_w C_w}} \quad (6.28)$$

由①式:

$$t_{pd} = \frac{RC_w L}{W} + RNC(1+P_{inv}) + \frac{R_w C_w L^2}{2N} + R_w C W L$$

$$\frac{\partial t_{pd}}{\partial W} = -\frac{RC_w L}{W^2} + R_w C L$$

$$\frac{\partial t_{pd}}{\partial W} = 0 \Rightarrow R_w C L = \frac{RC_w L}{W^2} \Rightarrow W = \sqrt{\frac{RC_w}{R_w C}} \quad (6.30)$$

由②式:

$$\frac{t_{pd}}{L} = \frac{R}{W} \left[C_w + \frac{N}{L} C W (1 + P_{inv}) \right] + R_w \left(\frac{C_w}{2N} + C W \right)$$

将(6.27)和(6.30)代入上式: $\frac{t_{pd}}{L} = (2 + \sqrt{2(1+P_{inv})}) \sqrt{RC R_w C_w}$

$$\text{代入 } P_{inv} = 0.5, \frac{t_{pd}}{L} = \frac{2 + \sqrt{3}}{\sqrt{5}} \sqrt{5RC R_w C_w} = 1.67 \sqrt{FQ_d R_w C_w} \quad (6.29)$$

$$C = C_w L + N C W (1 + P_{inv}) \leftarrow \text{总电容}$$

$$E = C V_{DD}^2$$

$$\therefore \frac{E}{L} = \left[C_w + \frac{N C W}{L} (1 + P_{inv}) \right] V_{DD}^2$$

代入(6.27)和(6.30)式, 有

$$\frac{E}{L} = \left[C_w + \frac{N C W}{L} (1 + P_{inv}) \right] V_{DD}^2 = C_w \left(1 + \sqrt{\frac{1 + P_{inv}}{2}} \right) V_{DD}^2 \stackrel{P_{inv}=0.5}{\approx} 1.87 C_w V_{DD}^2 \quad (6.31)$$