

- 11.2 Overflow for signed numbers only occurs when adding numbers with the same sign (positive or negative). The numbers overflow ( $V$ ) if the sign of the result  $Y$  does not match the sign of the inputs  $A$  and  $B$ :

$$V = A_{N-1}B_{N-1}\bar{Y}_{N-1} + \bar{A}_{N-1}\bar{B}_{N-1}Y_{N-1}$$

- 11.6 8 stages for 32-bit, 11 stages for 64-bit addition.

- 11.10


$$\begin{aligned} C_{\text{out}} &= \overline{(A \oplus B)\bar{C}} + \overline{(A \oplus B)A} \\ &= \overline{A\bar{B}\bar{C}} + \overline{A\bar{B}C} + \overline{A\bar{B}B} \\ &= \text{MAJ}(A, B, C) \end{aligned}$$

- 11.22 The following equations are a slight modification of EQ 10.50. Use the base case  $X_{1:1} = 1, W_{1:1} = 0$ .

$$\begin{aligned} X_{i:i} &= \overline{A_i \bar{A}_{i-1}} && \text{bitwise precomputation} \\ W_{i:i} &= \overline{A_i \bar{A}_{i-1}} \\ X_{i:j} &= X_{i:k} \cdot X_{k-1:j} && \text{group logic} \\ W_{i:j} &= W_{i:k} \cdot X_{k-1:j} + X_{i:k} \cdot W_{k-1:j} \\ Y_i &= W_{i:i} \cdot W_{i-1:1} && \text{output logic} \end{aligned}$$

- 12.2 The dimensions are (128 columns \* 1.3  $\mu\text{m}/\text{col}$  \* 1.1) x (128 rows \* 1.44  $\mu\text{m}/\text{row}$  \* 1.1) = 183  $\mu\text{m}$  x 203  $\mu\text{m}$ .

- 12.10

 

- 12.12 NAND ROMs use series rather than parallel transistors and one-cold rather than one-hot wordlines. They tend to be smaller than NOR ROMs because they do not require contacts between the series transistors, but they are also slower because of the series transistors.