
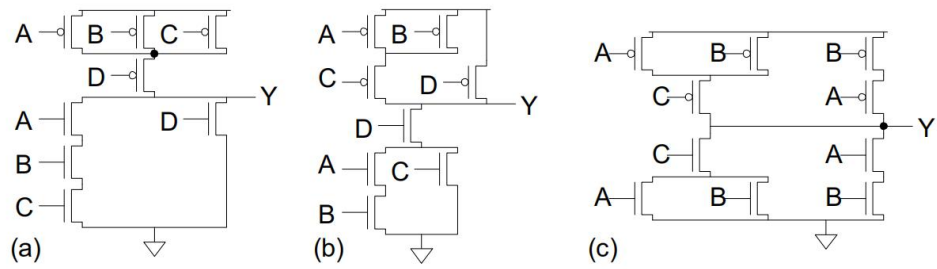



1.6

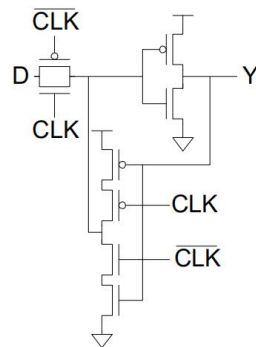

1.15 This latch is nearly identical save that the inverter and transmission gate feedback has been replaced by a tristate feedback gate.



1.18

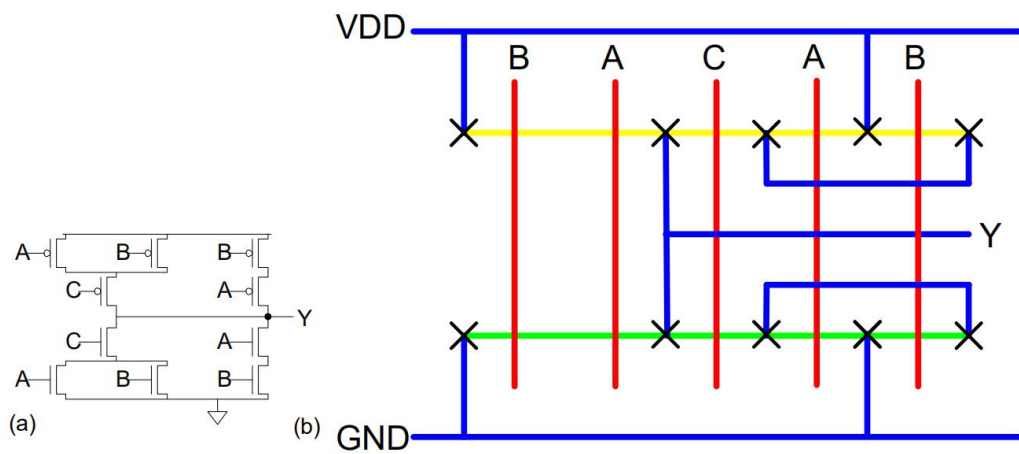

2.2 In (a), the transistor sees $V_{gs} = V_{DD}$ and $V_{ds} = V_{DS}$. The current is

$$I_{DS1} = \frac{\beta}{2} \left(V_{DD} - V_t - \frac{V_{DS}}{2} \right) V_{DS}$$

In (b), the bottom transistor sees $V_{gs} = V_{DD}$ and $V_{ds} = V_1$. The top transistor sees $V_{gs} = V_{DD} - V_1$ and $V_{ds} = V_{DS} - V_1$. The currents are

$$I_{DS2} = \beta \left(V_{DD} - V_t - \frac{V_1}{2} \right) V_1 = \beta \left((V_{DD} - V_1) - V_t - \frac{(V_{DS} - V_1)}{2} \right) (V_{DS} - V_1)$$

Solving for V_1 , we find

$$V_1 = (V_{DD} - V_t) - \sqrt{(V_{DD} - V_t)^2 - \left(V_{DD} - V_t - \frac{V_{DS}}{2} \right) V_{DS}}$$

Substituting V_1 into the I_{DS2} equation and simplifying gives $I_{DS1} = I_{DS2}$.

2.10 (a) $(1.2 - 0.3)^2 / (1.2 - 0.4)^2 = 1.26$ (26%)

(b)
$$\frac{e^{\frac{-0.3}{1.4 \cdot 0.026}}}{e^{\frac{-0.4}{1.4 \cdot 0.026}}} = 15.6$$

(c) $v_T = kT/q = 34$ mV;
$$\frac{e^{\frac{-0.3}{1.4 \cdot 0.034}}}{e^{\frac{-0.4}{1.4 \cdot 0.034}}} = 8.2$$
; note, however, that the total leakage

will normally be higher for both threshold voltages at high temperature.

2.16 Set the currents through the transistors equal and solve the nasty quadratic for V_{out} .

In region B, the nMOS is saturated and pMOS is linear:

$$\frac{\beta}{2}(V_{\text{in}} - V_t)^2 = \beta \left((V_{\text{in}} - V_{DD}) - \frac{(V_{\text{out}} - V_{DD})}{2} + V_t \right) (V_{\text{out}} - V_{DD})$$

$$V_{\text{out}} = (V_{\text{in}} + V_t) + \sqrt{(V_{\text{in}} + V_t)^2 - (V_{\text{in}} - V_t)^2 + V_{DD}(V_{DD} - 2V_{\text{in}} - 2V_t)}$$

In region D, the nMOS is linear and the pMOS is saturated:

$$\frac{\beta}{2}(V_{\text{in}} - V_{DD} + V_t)^2 = \beta \left(V_{\text{in}} - V_t - \frac{V_{\text{out}}}{2} \right) (V_{\text{out}})$$

$$V_{\text{out}} = (V_{\text{in}} - V_t) - \sqrt{(V_{\text{in}} - V_t)^2 - (V_{DD} - V_{\text{in}} - V_t)^2}$$

2.20 (a) 0; (b) $2|V_{tp}|$; (c) $|V_{tp}|$; (d) $V_{DD} - V_{tn}$