

Delay

Song Chen

Nov. 12, 2015

<http://staff.ustc.edu.cn/~songch/da-ug.htm>

Outline

- Delay
 - Gate
 - Wire (Interconnect)

Timing Optimization


- Architecture/Micro-architecture
 - Pipeline stages, number of execution units (parallelism), size of memories
 - Selected Algorithms, Technology, Memory access speed, Wire delay
- Logic level
 - Types of functional blocks (e.g., ripple carry vs. look-ahead adders), number of gate stages in the clock cycle, fan-in/fan-out of the gates
- Circuit-level
 - Transistor sizes, CMOS logic styles
- Layout-level
 - Floorplan, cell layouts, routing, etc.

Common Design Practice

- To **write** RTL code, **Simulate**
- **Synthesize** to check if the results are fast enough
 - Timing optimization at Logic, circuit, placement level.
 - If not: recode the RTL with more parallelism or pipelining, or changes the algorithm and repeats until the timing constraints are satisfied.
 - Timing analyzers are used to check the ***Timing closure***.
 - Without an understanding of the lower levels of abstraction where the synthesizer is working, a designer may have a difficult time achieving timing closure on a challenging system.

Delay Definitions

- t_{pdr}/t_{pdf} : *rising/falling **propagation** (maximum) delay*
 - From input to rising/falling output crossing $V_{DD}/2$
- t_{cdr}/t_{cdf} : *rising/falling **contamination** (minimum) delay*
 - From input to falling output crossing $V_{DD}/2$
- t_{pd}/t_{cd} : *average propagation delay*
 - $t_{pd} = (t_{pdr} + t_{pdf})/2$
- t_r : *rise time*
 - From output crossing $0.2 V_{DD}$ to $0.8 V_{DD}$
- t_f : *fall time*
 - From output crossing $0.8 V_{DD}$ to $0.2 V_{DD}$


 


Delay Estimation

- We would like to be able to easily estimate delay
 - Not as accurate as simulation
 - But easier to ask “What if?”
- Use RC delay models to estimate delay
 - C = total capacitance on output node
 - Use *effective resistance* R
 - So that $t_{pd} = RC$
- Characterize transistors by finding their effective R
 - Depends on average current as gate switches

RC Delay Model

 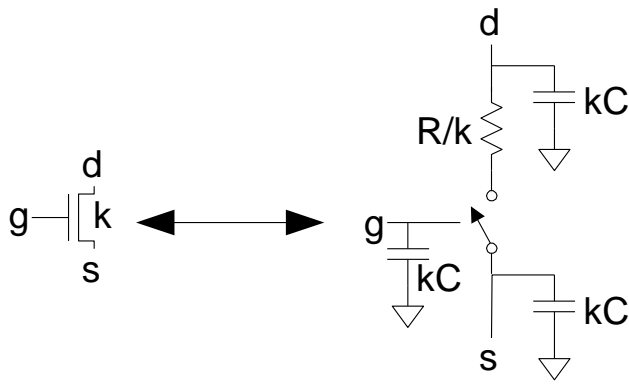- Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- Capacitance proportional to width
- Resistance inversely proportional to width




RC Values

- Capacitance
 - $C = C_g = C_s = C_d = 2 \text{ fF}/\mu\text{m}$ of gate width in $0.6 \mu\text{m}$
 - Gradually decline to $1 \text{ fF}/\mu\text{m}$ in nanometer techs.
- Resistance
 - $R \approx 6 \text{ K}\Omega \cdot \mu\text{m}$ in $0.6 \mu\text{m}$ process
 - Improves with shorter channel lengths
- Unit transistors
 - May refer to minimum contacted device ($4/2 \lambda$)
 - Or maybe $1 \mu\text{m}$ wide device
 - Doesn't matter as long as you are consistent

Inverter Delay Estimate

 
- Estimate the delay of a fanout-of-1 inverter



$$d = 6RC$$

 
Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).



3-input NAND Caps

 - Annotate the 3-input NAND gate with gate and diffusion capacitance.




Elmore Delay

- ON transistors look like resistors
- Pullup or pulldown network modeled as *RC ladder*
- Elmore delay of RC ladder




$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$
 
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$




 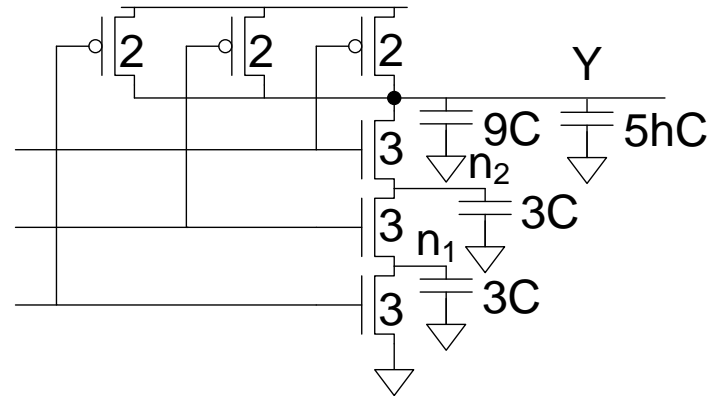 Example: 3-input NAND

- Estimate worst-case rising and falling delay of 3-input NAND driving h identical gates.



$$t_{pdr} = (15 + 5h)RC$$

 



$$\begin{aligned} t_{pdf} &= (3C)(R/3) + (3C)(R/3 + R/3) + [(9 + 5h)C](R/3 + R/3 + R/3) \\ &= (12 + 5h)RC \end{aligned}$$

Delay Components

- Delay has two parts
 - *Parasitic delay*
 - 9 or 11 RC
 - Independent of load
 - *Effort delay*
 - 5h RC
 - Proportional to load capacitance

Contamination Delay

 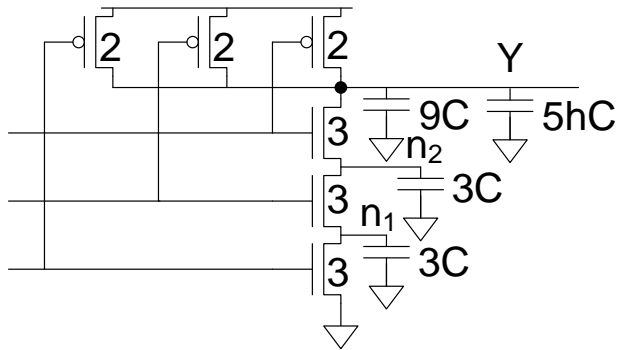
- Best-case (contamination) delay can be substantially less than propagation delay.
- Ex: If all three inputs fall simultaneously



$$t_{cdr} = \left[(9 + 5h)C \right] \left(\frac{R}{3} \right) = \left(3 + \frac{5}{3}h \right) RC$$

Diffusion Capacitance

 - We assumed contacted diffusion on every s / d.
- Good layout minimizes diffusion area
- Ex: NAND3 layout shares one diffusion contact
 - Reduces output capacitance by $2C$
 - Merged uncontacted diffusion might help too



Timing Analysis Delay Models

- Slope-Based Linear Model
 - $\text{delay_rise} = \text{intrinsic_rise} + \text{rise_resistance} \times \text{capacitance} + \text{slope_rise} \times \text{delay_previous}$
 - $\text{delay_fall} = \text{intrinsic_fall} + \text{fall_resistance} \times \text{capacitance} + \text{slope_fall} \times \text{delay_previous}$
- Nonlinear Delay Model: Two-dimensional interpolation
 - Look up the delay from a table based on the **load capacitance** and the **input slope**
- Current Source Model
 - Express the **output DC current** as a **nonlinear function** of the input and output **voltages** of the cell
 - Analyzer numerically integrates the output current to find the **voltage** as a **function of time** into an arbitrary RC network and to solve for the **propagation delay**.

Wire/Interconnect


- Introduction
- Interconnect Modeling
 - Wire Resistance
 - Wire Capacitance
- Wire RC Delay
- Crosstalk
- Wire Engineering
- Repeaters

Introduction

- Chips are mostly made of wires called *interconnect*
 - Transistors are little things under the wires
 - Many layers of wires
- Wires are as important as transistors
 - Speed
 - Power
 - Noise
- Alternating layers run orthogonally

Wire Geometry

 
- Pitch = $w + s$
- Aspect ratio: $AR = t/w$
 - Old processes had $AR \ll 1$
 - Modern processes have $AR \approx 2$
 - Pack in many skinny wires



Layer Stack


- AMI 0.6 μm process has 3 metal layers
 - M1 for within-cell routing
 - M2 for vertical routing between cells
 - M3 for horizontal routing between cells
- Modern processes use 6-10+ metal layers
 - M1: thin, narrow ($< 3\lambda$)
 - High density cells
 - Mid layers
 - Thicker and wider, (density vs. speed)
 - Top layers: thickest
 - For V_{DD} , GND, clk

Example

 

Intel 90 nm Stack

[Thompson02]

 


Intel 45 nm Stack

[Moon08]


Interconnect Modeling

 - Current in a wire is analogous to current in a pipe
 - Resistance: narrow size impedes flow
 - Capacitance: trough under the leaky pipe must fill first
 - Inductance: paddle wheel inertia opposes changes in flow rate
 - Negligible for most wires



Lumped Element Models

 - Wires are a distributed system
 - Approximate with lumped element models




- 3-segment π -model is accurate to 3% in simulation
- L-model needs 100 segments for same accuracy!
- Use single segment π -model for Elmore delay

Wire Resistance

- $\rho = \text{resistivity } (\Omega \cdot \text{m})$

$$R =$$

 - $R_{\square} = \text{sheet resistance } (\Omega / \square)$
 - \square is a dimensionless unit(!)
- Count number of squares
 - $R = R_{\square} * (\# \text{ of squares})$



Choice of Metals

- Until 180 nm generation, most wires were aluminum
- Contemporary processes normally use copper
 - Cu atoms diffuse into silicon and damage FETs
 - Must be surrounded by a diffusion barrier

Metal	Bulk resistivity ($\mu\Omega \cdot \text{cm}$)
Silver (Ag)	1.6
Copper (Cu)	1.7
Gold (Au)	2.2
Aluminum (Al)	2.8
Tungsten (W)	5.3
Titanium (Ti)	43.0

Contacts Resistance


- Contacts and vias also have 2-20 Ω
 - Depending on the contacted materials and size of the contact
- Use many contacts for lower R
 - Many small contacts for current crowding around periphery



Copper Issues


- Copper wires diffusion barrier has high resistance
- Copper is also prone to *dishing* polishing
- Effective resistance is higher
 
$$R = \frac{\rho}{(t - t_{\text{dish}} - t_{\text{barrier}})} \frac{l}{(w - 2t_{\text{barrier}})}$$



Wire Capacitance

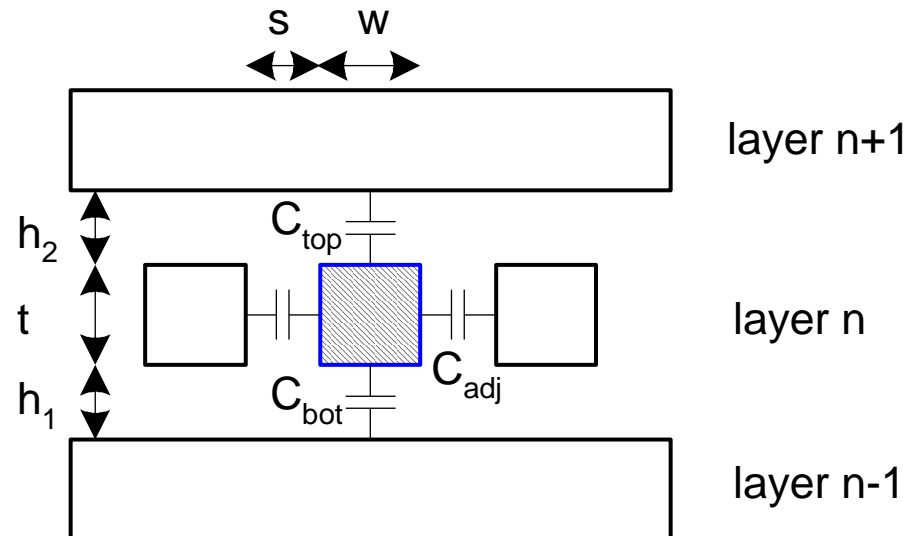- Wire has capacitance per unit length
 - To neighbors
 - To layers above and below
- $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$




Capacitance Trends

- Parallel plate equation: $C = \epsilon_{\text{ox}} A/d$
 - Wires are not parallel plates, but obey trends
 - Increasing area (w, t) increases capacitance
 - Increasing distance (s, h) decreases capacitance
- Dielectric constant
 - $\epsilon_{\text{ox}} = k\epsilon_0$
 - $\epsilon_0 = 8.85 \times 10^{-14} \text{ F/cm}$
 - $k = 3.9$ for SiO_2
- Processes are starting to use low-k dielectrics
 - $k \approx 3$ (or less) as dielectrics use air pockets

M2 Capacitance Data

 - Typical dense wires have $\sim 0.2 \text{ fF}/\mu\text{m}$
 - *Compare to 1-2 fF/ μm for gate capacitance*




Capacitance of metal2
(180nm) line as a function
of width and spacing


Wire RC Delay

- Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 1 mm wire. Assume wire capacitance is $0.2 \text{ fF}/\mu\text{m}$ and that a unit-sized nMOS transistor has $R = 10 \text{ K}\Omega$ and $C = 0.1 \text{ fF}$.

– $t_{pd} =$

 

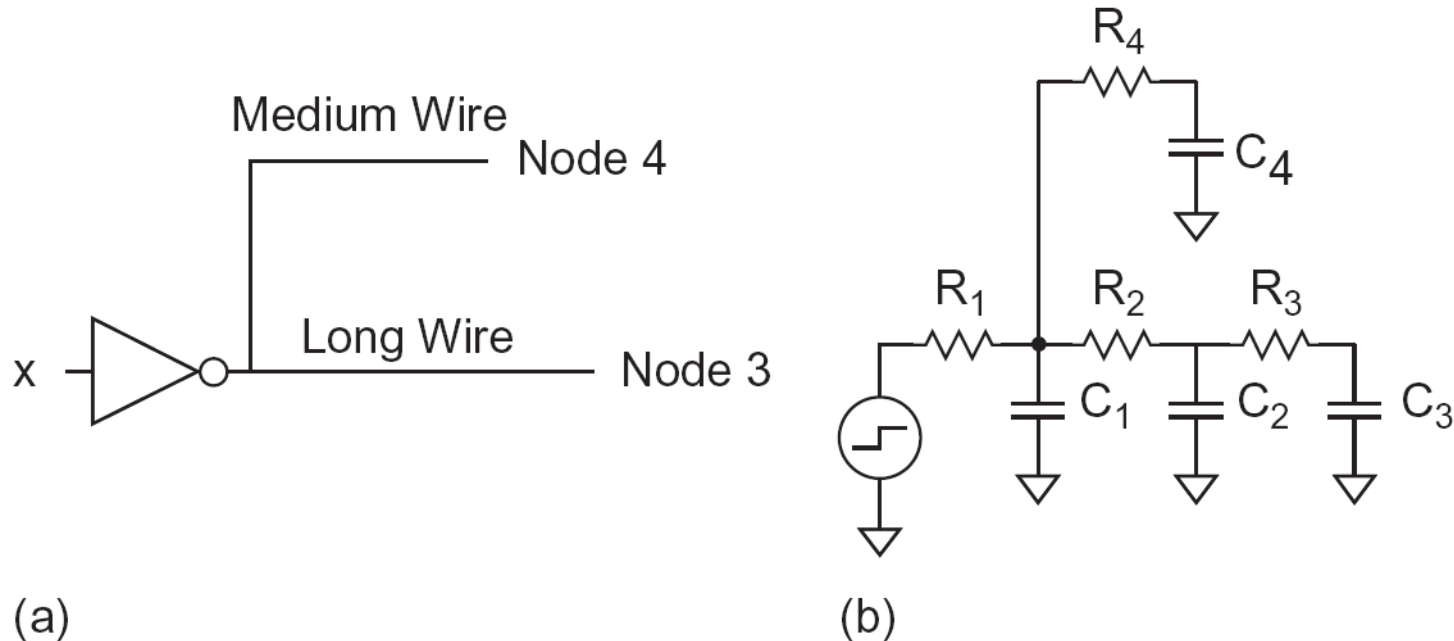Interconnect Modeling with RC tree (Elmore Delay)



$$T_{D_3} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 + R_1 C_4$$


$$T_{D_4} = R_1 C_1 + R_1 (C_2 + C_3) + (R_1 + R_4) C_4$$

Crosstalk

- A capacitor does not like to change its voltage instantaneously.
- A wire has high capacitance to its neighbor.
 - When the neighbor switches from 1- \rightarrow 0 or 0- \rightarrow 1, the wire tends to switch too.
 - Called capacitive *coupling* or *crosstalk*.
- Crosstalk effects
 - Noise on nonswitching wires
 - Increased delay on switching wires

Crosstalk Delay

 - Assume layers above and below on average are quiet
 - Second terminal of capacitor can be ignored
 - Model as $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$
- A Switches: Effective C_{adj} depends on behavior of neighbors
 - *Miller effect*




B	ΔV	$C_{\text{eff(A)}}$	MCF
Constant			
Switching with A			
Switching opposite A			

Crosstalk Noise

- Crosstalk causes noise on non-switching wires
- If victim is floating:
 - model as capacitive voltage divider
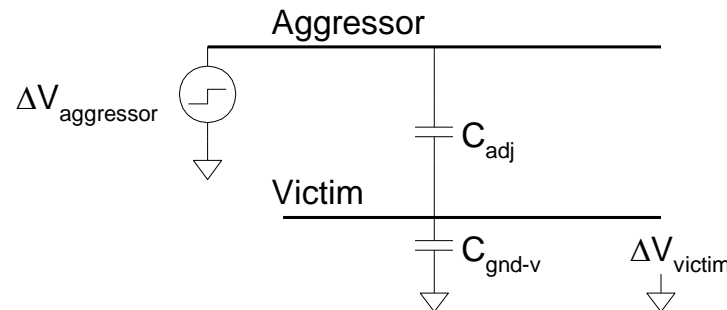
$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \Delta V_{aggressor}$$




Driven Victims

- Usually victim is driven by a gate that fights noise
 - Noise depends on relative resistances
 - Victim driver is in linear region, agg. in saturation
 - If sizes are same, $R_{\text{aggressor}} = 2-4 \times R_{\text{victim}}$


$$\Delta V_{\text{victim}} = \frac{C_{\text{adj}}}{C_{\text{gnd-v}} + C_{\text{adj}}} \frac{1}{1+k} \Delta V_{\text{aggressor}}$$
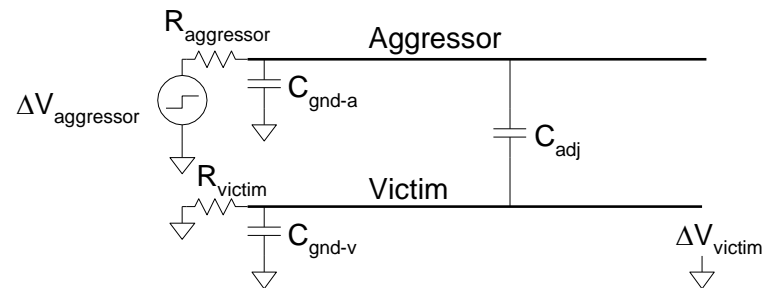
$$k = \frac{\tau_{\text{aggressor}}}{\tau_{\text{victim}}} = \frac{R_{\text{aggressor}} (C_{\text{gnd-a}} + C_{\text{adj}})}{R_{\text{victim}} (C_{\text{gnd-v}} + C_{\text{adj}})}$$



Coupling Waveforms

 - Simulated coupling for $C_{\text{adj}} = C_{\text{victim}}$






Noise Implications

- *So what* if we have noise?
- If the noise is less than the noise margin, nothing happens
- Static CMOS logic will eventually settle to correct output even if disturbed by large noise spikes
 - But glitches cause extra delay
 - Also cause extra power from false transitions
- Memories and other sensitive circuits also can produce the wrong answer



Wire Engineering

 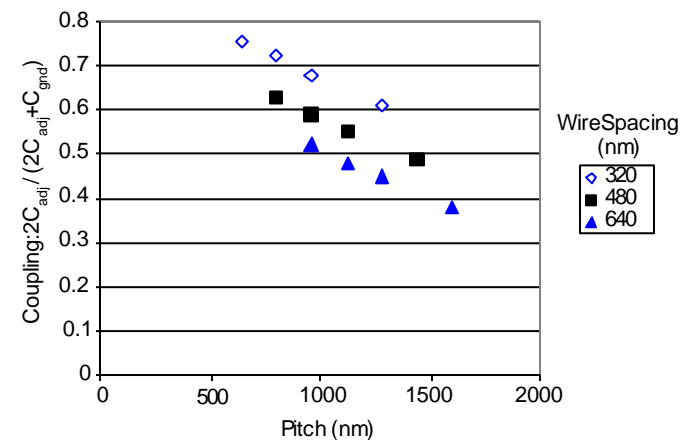 - Goal: achieve delay, area, power goals with acceptable noise
- Degrees of freedom:
 - Width
 - Spacing
 - Layer
 - Shielding




Repeaters

  - R and C are proportional to l
- RC delay is proportional to l^2
 - Unacceptably great for long wires
- Break long wires into N shorter segments
 - Drive each one with an inverter or buffer



Repeater Design

 - How many repeaters should we use?
- How large should each one be?
- Equivalent Circuit
 - Wire length l/N
 - Wire Capacitance $C_w * l/N$, Resistance $R_w * l/N$
 - Inverter width W (nMOS = W , pMOS = $2W$)
 - Gate Capacitance $C' * W$, Resistance R/W



Repeater Results

- Write equation for Elmore Delay

$$t_{pd} = N \left[\frac{R}{W} \left(C_w \frac{l}{N} + CW(1 + p_{inv}) \right) + R_w \frac{l}{N} \left(\frac{C_w}{2} \frac{l}{N} + CW \right) \right]$$

- Differentiate with respect to W and N
- Set equal to 0, solve

$$\frac{l}{N} = \sqrt{\frac{2RC'}{R_w C_w}}$$

~40 ps/mm

$$\frac{t_{pd}}{l} = (2 + \sqrt{2}) \sqrt{RC'R_w C_w}$$

in 65 nm process

$$W = \sqrt{\frac{RC_w}{R_w C'}}$$

Repeater Energy

- Energy / length $\approx 1.87C_w V_{DD}^2$
 - 87% premium over unpeated wires
 - The extra power is consumed in the large repeaters
- If the repeaters are downsized for minimum EDP:
 - Energy premium is only 30%
 - Delay increases by 14% from min delay

Reference

- Reference [4]. Chapter 4.3, Chapter 6