

Verilog Basics and RTL Simulation

Song Chen

Dept. of Electronic Science & Technology, USTC

September 24, 2015

<http://staff.ustc.edu.cn/~songch/da-ug.htm>


Outline

- Verilog Basics
 - Data Type
 - Structural Verilog
 - Simple Behavior
- Verilog Execution Semantics
 - Driven by simulation
 - Explained using event queues

Bit-vector is the only data type in Verilog

A bit can take on one of four values

Value	Meaning
0	Logic zero
1	Logic one
X	Unknown logic value
Z	High impedance, floating





An X bit might be a 0, 1, Z, or in transition. We can set bits to be X in situations where we don't care what the value is. This can help catch bugs and improve synthesis quality.

“wire” is used to denote a hardware net (connection)


```
wire [15:0] instruction;  
wire [15:0] memory_req;  
wire [ 7:0] small_net;
```

  Absolutely no type
safety when
connecting nets!



Bit literals

4' b10_11

 


We'll learn how to
actually assign literals
to nets a little later

- Binary literals
 - 8' b0000_0000
 - 8' b0xx0_1xx1
- Hexadecimal literals
 - 32' h0a34_def1
 - 16' haxxx
- Decimal literals
 - 32' d42

Outline

- Verilog Basics
 - Data Type
 - Structural Verilog
 - Simple Behavior
- Verilog Execution Semantics
 - Driven by simulation
 - Explained using event queues

 A Verilog module has a name and a port list




```
module adder( A, B, cout, sum );  
    input  [3:0] A;  
    input  [3:0] B;  
    output          cout;  
    output [3:0] sum;  
  
    // HDL modeling of  
    // adder functionality  
  
endmodule
```

Ports must have a direction (or be bidirectional) and a bitwidth

Note the semicolon at the end of the port list!

Alternate syntax

 


Traditional Verilog-1995 Syntax

```
module adder( A, B, cout, sum );  
  input  [3:0] A;  
  input  [3:0] B;  
  output                cout;  
  output [3:0] sum;
```

ANSI C Style Verilog-2001 Syntax

```
module adder( input  [3:0] A,  
              input  [3:0] B,  
              output                cout,  
              output [3:0] sum );
```


A module can instantiate other modules

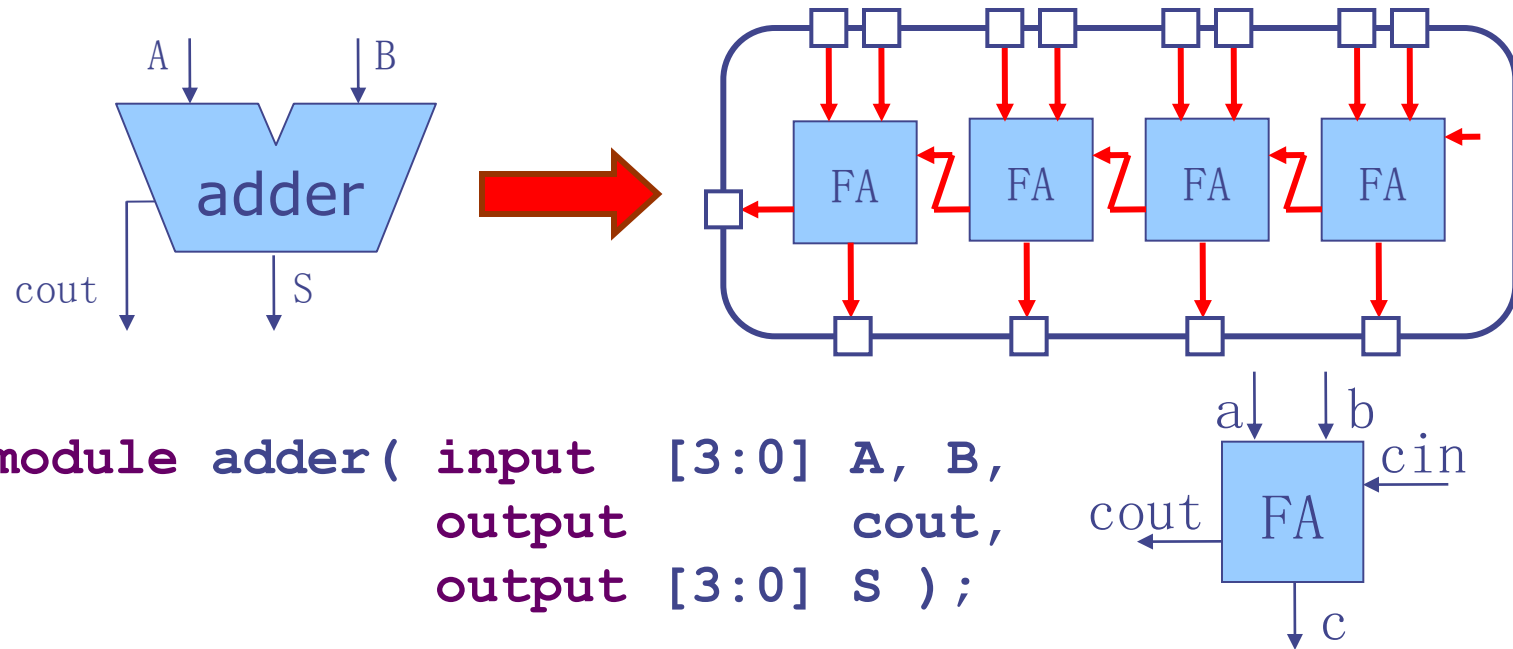

```
module adder( input  [3:0] A, B,  
              output   cout,  
              output  [3:0] S );
```

```
    wire c0, c1, c2;
```

```
    FA fa0( ... );
```

```
    FA fa1( ... );
```

```
    FA fa2( ... );
```


```
    FA fa3( ... );
```

```
endmodule
```

```
module FA( input  a, b, cin  
           output cout, sum );  
    // HDL modeling of 1 bit  
    // full adder functionality  
endmodule
```

```
assign {cout, s} = A + B;
```

Connecting modules

 

```
module adder( input  [3:0] A, B,  
              output   cout,  
              output [3:0] S );
```

```
    wire c0, c1, c2;
```

```
    FA fa0( A[0], B[0], 1'b0, c0, S[0] );
```

```
    FA fa1( A[1], B[1], c0, c1, S[1] );
```

```
    FA fa2( A[2], B[2], c1, c2, S[2] );
```

```
    FA fa3( A[3], B[3], c2, cout, S[3] );
```

```
endmodule
```

Carry Chain

Alternative syntax

Connecting ports by ordered list

```
FA fa0( A[0], B[0], 1'b0, c0, S[0] );
```

Connecting ports by name (compact)

```
FA fa0( .a(A[0]), .b(B[0]),  
        .cin(1'b0), .cout(c0), .sum(S[0]) );
```

Argument order does not matter when ports are connected by name

```
FA fa0  
( .a      (A[0]),  
  .cin    (1'b0),  
  .b      (B[0]),  
  .cout   (c0),  
  .sum    (S[0]) );
```

Connecting ports by name
yields clearer and less
buggy code.

Outline


- Verilog Basics
 - Data Type
 - Structural Verilog
 - Simple Behavior
- Verilog Execution Semantics
 - Driven by simulation
 - Explained using event queues

A module's behavior can be described in many different ways but it should not matter from outside

Example: 4-1 multiplexor

mux4: Gate-level structural Verilog

```
module mux4(input a,b,c,d, input [1:0] sel, output out);  
  wire [1:0] sel_b;  
  not not0( sel_b[0], sel[0] );  
  not not1( sel_b[1], sel[1] );  
  
  wire n0, n1, n2, n3;  
  and and0( n0, c, sel[1] );  
  and and1( n1, a, sel_b[1] );  
  and and2( n2, d, sel[1] );  
  and and3( n3, b, sel_b[1] );  
  
  wire x0, x1;  
  nor nor0( x0, n0, n1 );  
  nor nor1( x1, n2, n3 );  
  
  wire y0, y1;  
  or or0( y0, x0, sel[0] );  
  or or1( y1, x1, sel_b[0] );  
  nand nand0( out, y0, y1 );  
endmodule
```

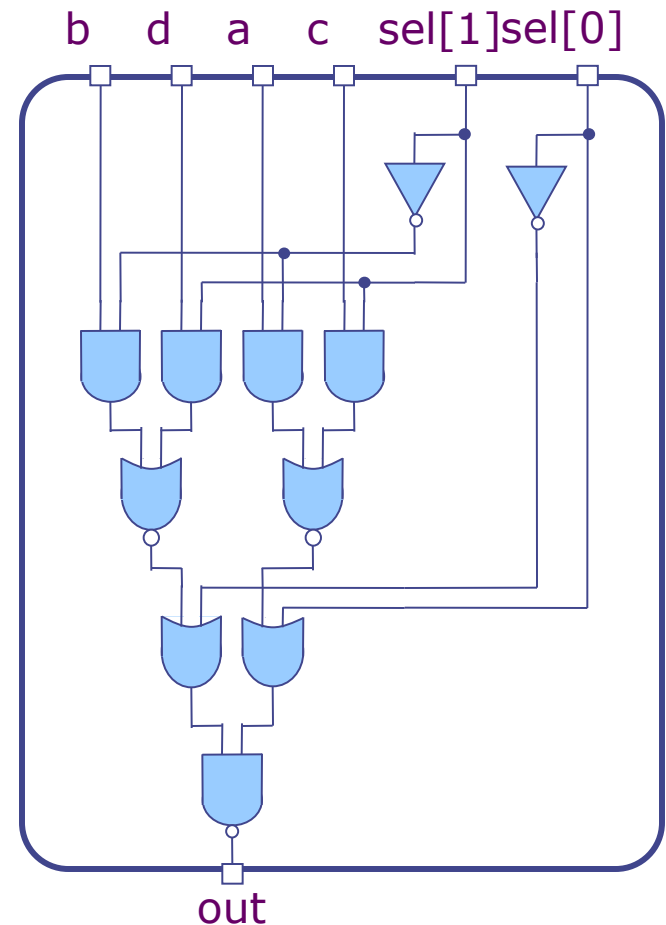


mux4: Using continuous assignments

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    wire out, t0, t1;
    assign out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    assign t1  = ~( (sel[1] & d) | (~sel[1] & b) );
    assign t0  = ~( (sel[1] & c) | (~sel[1] & a) );

endmodule
```

Language defined operators

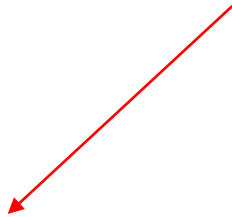

The order of these continuous assignment statements does not matter.
They essentially happen in parallel!

mux4: Behavioral style

```
// Four input multiplexer
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    assign out = ( sel == 0 ) ? a :
                  ( sel == 1 ) ? b :
                  ( sel == 2 ) ? c :
                  ( sel == 3 ) ? d : 1'bx;

endmodule
```

If input is undefined
we want to propagate
that information.

mux4: Using “always block”

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
```

Motivated by simulation



```
    reg out, t0, t1;
```

```
    always @( a or b or c or d or sel )
```

```
    begin
```

```
        t0 = ~( (sel[1] & c) | (~sel[1] & a) );
```

```
        t1 = ~( (sel[1] & d) | (~sel[1] & b) );
```

```
        out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
```

```
    end
```

```
endmodule
```

The order of these procedural
assignment statements DOES matter.
They essentially happen sequentially!

“Always blocks” permit more advanced sequential idioms

```
module mux4( input  a,b,c,d
             input [1:0] sel,
             output out );

  reg out;
  always @( * )
  begin
    if ( sel == 2'd0 )
      out = a;
    else if ( sel == 2'd1 )
      out = b;
    else if ( sel == 2'd2 )
      out = c;
    else if ( sel == 2'd3 )
      out = d;
    else
      out = 1'bx;
  end
endmodule
```

```
module mux4( input  a,b,c,d
             input [1:0] sel,
             output out );

  reg out;
  always @( * )
  begin
    case ( sel )
      2'd0 : out = a;
      2'd1 : out = b;
      2'd2 : out = c;
      2'd3 : out = d;
      default : out = 1'bx;
    endcase
  end
endmodule
```

Typically we will use always blocks only to describe sequential circuits

What happens if the case statement is not complete?

```
module mux3( input  a, b, c
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
        endcase
    end

endmodule
```

If sel = 3, mux will output
the previous value!

What have we created?

What happens if the case statement is not complete?

```
module mux3( input  a, b, c
             input [1:0] sel,
             output out );
```

```
    reg out;
```

```
    always @( * )
```

```
    begin
```

```
        case ( sel )
```

```
            2'd0 : out = a;
```

```
            2'd1 : out = b;
```

```
            2'd2 : out = c;
```

```
            default : out = 1'bx;
```

```
        endcase
```

```
    end
```

```
endmodule
```

We CAN prevent creating
state with a default
statement

Parameterized mux4

```
module mux4 #( parameter WIDTH = 1 )  
    ( input[WIDTH-1:0]  a, b, c, d  
      input [1:0] sel,  
      output[WIDTH-1:0] out );
```

default value

```
    wire [WIDTH-1:0] out, t0, t1;  
  
    assign t0  = (sel[1]? c : a);  
    assign t1  = (sel[1]? d : b);  
    assign out = (sel[0]? t0: t1);  
endmodule
```

Parameterization is a good
practice for reusable modules
Writing a mux n is challenging

Instantiation Syntax


```
mux4#(32) alu_mux  
    ( .a (op1),  
      .b (op2),  
      .c (op3),  
      .d (op4),  
      .sel (alu_mux_sel),  
      .out (alu_mux_out) );
```

Verilog Registers “reg”


- Wires are line names – they do not represent storage and can be assigned only once
- Regs are imperative variables (as in C):
 - “nonblocking” assignment $r \leq v$
 - can be assigned multiple times and holds values between assignments

flip-flops
 
```
module FF0 (input clk, input d,
            output reg q);
always @( posedge clk )
begin
    q <= d;
end
endmodule
```



 
```
module FF (input clk, input d,
            input en, output reg q);
always @( posedge clk )
begin
    if ( en )
        q <= d;
end
endmodule
```



flip-flops with reset

```
always @( posedge clk)
begin
    if (~resetN)
        Q <= 0;
    else if ( enable )
        Q <= D;
end
synchronous reset
```
 
```
always @( posedge clk or
           negedge resetN)
begin
    if (~resetN)
        Q <= 0;
    else if ( enable )
        Q <= D;
end
asynchronous reset
```



What is the difference?

Latches versus flip-flops

```
module latch
(
    input  clk,
    input  d,
    output reg q
);

    always @( clk or d )
    begin
        if ( clk )
            q <= d;
    end
endmodule
```

```
module flipflop
(
    input  clk,
    input  d,
    output reg q
);

    always @( posedge clk )
    begin
        q <= d;
    end
endmodule
```

Edge-triggered
always block



Register

```
module register#(parameter WIDTH = 1)
(
    input  clk,
    input  [WIDTH-1:0] d,
    input  en,
    output [WIDTH-1:0] q
);

    always @( posedge clk )
    begin
        if (en)
            q <= d;
    end

endmodule
```

Register in terms of Flipflops

```
module register2
( input  clk,
  input  [1:0] d,
  input  en,
  output [1:0] q );

  always @(posedge clk)
  begin
    if (en)
      q <= d;
  end

endmodule
```

```
module register2
( input  clk,
  input  [1:0] d,
  input  en,
  output [1:0] q
);
  FF ff0 (.clk(clk), .d(d[0]),
          .en(en), .q(q[0]));

  FF ff1 (.clk(clk), .d(d[1]),
          .en(en), .q(q[1]));

endmodule
```

Do they behave the same?

yes

Register file with 2 combinational read ports and 1 write port

```
module smipsProcDpathRegfile
( input      clk,
  input  [ 4:0] raddr0,  // Read 0 address (combinational input)
  output [31:0] rdata0,  // Read 0 data (combinational on raddr)
  input  [ 4:0] raddr1,  // Read 1 address (combinational input)
  output [31:0] rdata1,  // Read 1 data (combinational on raddr)
  input      wen_p,      // Write enable (sample on rising clk edge)
  input  [ 4:0] waddr_p,  // Write address (sample on rising clk edge)
  input  [31:0] wdata_p   // Write data (sample on rising clk edge));

  // We use an array of 32 bit register for the regfile itself
  reg [31:0] registers[31:0];

  // Combinational read ports
  assign rdata0 = registers[raddr0];
  assign rdata1 = registers[raddr1];

  // Write port is active only when wen is asserted
  always @( posedge clk )
    if ( wen_p )
      registers[waddr_p] <= wdata_p;
endmodule
```

Static Elaboration: Generate

```
module register#(parameter WIDTH = 1)
( input  clk,
  input  [WIDTH-1:0] d,
  input  en,
  output [WIDTH-1:0] q
);
```

genvars disappear after
static elaboration



```
genvar i;
```

```
generate
```

```
for (i = 0; i < WIDTH; i = i + 1)
```

```
begin: regE
```

```
    FF ff(.clk(clk), .d(d[i]), .en(en), .q(q[i]));
```

```
end
```


```
endgenerate
```

```
endmodule
```

Generated names will have
regE[i]. prefix



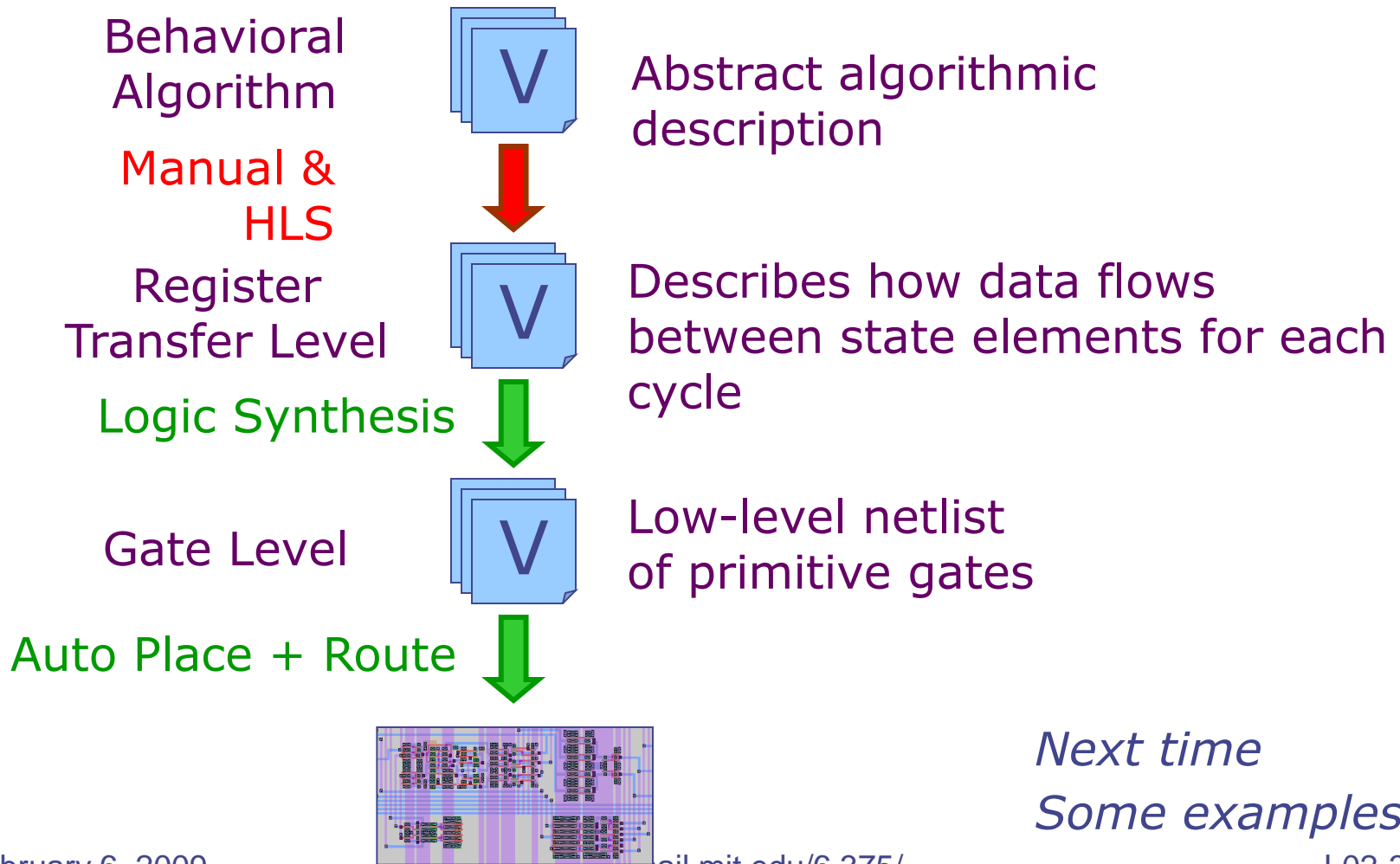Three abstraction levels for functional descriptions



Guidelines for writing synthesizable (合成可能) Verilog

- Combinational logic:
 - Use continuous assignments (`assign`)
`assign C_in = B_out + 1;`
 - Use `always@(*)` blocks with blocking assignments (`=`)


```
always @(*)
begin
    out = 2'd0;
    if (in1 == 1)
        out = 2'd1;
    else if (in2 == 1)
        out = 2'd2;
end
```
- Sequential logic:
 - Use `always @(posedge clk)` and non-blocking assignments (`<=`)

```
always @(posedge clk)
    C_out <= C_in;
```
 - Use only positive-edge triggered flip-flops for state
 - Do not assign the same variable from more than one `always` block
- Only leaf modules should have functionality; use higher-level modules only for wiring together sub-modules

An example

```
module non_block #(parameter WIDTH = 4)
  (input clk,
   input [WIDTH-1:0] A_in,
   output reg [WIDTH-1:0] C_out = 0);

 
  reg [WIDTH-1:0] A_out, B_out;
  always @( posedge clk )
  begin
    A_out <= A_in;
    B_out <= A_out + 1;
    C_out <= B_out + 1;
  end
endmodule
```



The order of non-blocking assignments does not matter!

Another style – multiple `always` blocks
 
```
reg [WIDTH-1:0] A_out, B_out;  
  
always @( posedge clk )  
    A_out <= A_in;  
  
always @( posedge clk )  
    B_out <= A_out + 1;  
  
always @( posedge clk )  
    C_out <= B_out + 1;
```




Does it have the same functionality?

Yes. But why?

Need to understand something about Verilog execution semantics

Yet another style – blocking assignments

 
```
reg [WIDTH-1:0] A_out, B_out;  
always @( posedge clk )  
begin  
    A_out = A_in;  
    B_out = A_out + 1;  
    C_out = B_out + 1;  
end
```



Does it have the same functionality?

Not even close!
 
```
always @( posedge clk )  
begin  
    C_out = B_out + 1;  
    B_out = A_out + 1;  
    A_out = A_in;  
end
```



Test module structure (test bench)

Once a design module is completed it must be tested
Functionality of the design module can be tested by
applying stimulus and checking results.

```
Module <test module name>;  
// Data type declaration  
// Instantiate module (call the module that is going to be tested)  
// Apply the stimulus  
// Display results  
endmodule
```

Test bench for the adder (Synopsys vcs)

```
module adder_test;
reg [3:0] A, B;    // reg type for input
wire [3:0] sum;    // wire type for output
wire cout;
adder adder_a(.cout(cout),.A(A),.B(B),.s(sum));
initial
begin
    $vcdpluson(0);
    $monitor("%t A = %h B = %h, c_out=%b, sum = %h", $time, A, B,
cout, sum);
    A <= 4'b0000; B <= 4'b0000;
    #10 A <= 4'b1100; B <= 4'b0111; #10 A <= 4'b0000; B <= 4'b0111;
    #10 A <= 4'b1100; B <= 4'b1011; #10 A <= 4'b0110; B <= 4'b0101;
    #10 A <= 4'b1110; B <= 4'b0011; #10
    $finish;
end
//high-level descriptions
endmodule
```

Verilog execution semantics

- Driven by simulation
- Explained using event queues

Execution semantics of Verilog - 1

```
wire A_in, B_in, C_in;  
reg  A_out, B_out, C_out;
```

```
always @( posedge clk )  
    A_out <= A_in;
```

```
assign B_in = A_out + 1;
```

```
always @( posedge clk )  
    B_out <= B_in;
```

```
assign C_in = B_out + 1;
```

```
always @( posedge clk )  
    C_out <= C_in;
```

A


1

B

2

C

Active Event Queue

 

On clock edge all those events which are sensitive to the clock are added to the active event queue in any order!

Execution semantics of Verilog - 2

```
wire A_in, B_in, C_in;  
reg  A_out, B_out, C_out;
```

```
always @( posedge clk )  
    A_out <= A_in;
```

A

```
assign B_in = A_out + 1;
```

1

```
always @( posedge clk )  
    B_out <= B_in;
```

B


```
assign C_in = B_out + 1;
```

2

```
always @( posedge clk )  
    C_out <= C_in;
```

C

Active Event Queue

 

A evaluates and as a consequence 1 is added to the event queue

Execution semantics of Verilog -3

```
wire A_in, B_in, C_in;  
reg  A_out, B_out, C_out;
```

```
always @( posedge clk )  
    A_out <= A_in;
```

A

```
assign B_in = A_out + 1;
```

1

```
always @( posedge clk )  
    B_out <= B_in;
```

B


```
assign C_in = B_out + 1;
```

2

```
always @( posedge clk )  
    C_out <= C_in;
```

C

Active Event Queue

 

Event queue is emptied
before we go to next
clock cycle

Non-blocking assignment

- Within a “clock cycle” all RHS variables are read first and all the LHS variables are updated together at the end of the clock cycle
- Consequently, two event queues have to be maintained – one keeps the computations to be performed while the other keeps the variables to be updated

Non-blocking assignments require two event queues

```
wire A_in, B_in, C_in;  
reg  A_out, B_out, C_out;
```

```
always @( posedge clk )  
    A_out <= A_in;
```

A

```
assign B_in = A_out + 1;
```

1

```
always @( posedge clk )  
    B_out <= B_in;
```

B


```
assign C_in = B_out + 1;
```

2


```
always @( posedge clk )  
    C_out <= C_in;
```

C

Active Event Queue

 


Non-Blocking Queue

 

Variables in RHS of always blocks are not updated until all inputs (e.g. LHS + dependencies) are evaluated

Blocking assignments have a sequential language like semantics
 
```
wire A_in, B_in, C_in;  
reg  A_out, B_out, C_out;  
  
always @( posedge clk )  
begin  
    A_out = A_in;  
    B_out = A_out + 1;  
    C_out = B_out + 1;  
end
```



Behavioral Verilog is richer

- Characterized by heavy use of sequential blocking statements in large always blocks
- Many constructs are **not synthesizable** but can be useful for **behavioral modeling** and **test benches**
 - Data dependent **for** and **while** loops
 - Additional behavioral datatypes: **integer**, **real**
 - Magic initialization blocks: **initial**
 - Magic delay statements: **#<delay>**
 - System calls: **\$display**, **\$monitor**, **\$finish**

A simple summary

- Define a Module

```
module name( port list);  
    // HDL modeling of functionality  
    assign ... // data flow assignment  
    always @ (posedge clk) ... // sequential  
    always @ (*) ... // combinational  
    instantiation of lower level modules ...  
    task and function  
endmodule
```

Take away points

- Follow the simple guidelines to write synthesizable Verilog
- Parameterized models provide the foundation for reusable libraries of components
- Use explicit state to prevent unwanted state inference and to more directly represent the desired hardware
- Begin your RTL design by identifying the external interface and then move on to partition your design into the **memories**, **datapaths**, and **control logic**