

Timing

(时序)

Song Chen

October 15, 2015

<http://staff.ustc.edu.cn/~songch/da-ug.htm>

Outline

- ❑ Sequencing
- ❑ Sequencing Element Design
- ❑ Max and Min-Delay
- ❑ Clock Skew
- ❑ Time Borrowing
- ❑ Two-Phase Clocking
- ❑ Timing Analysis


Sequencing

❑ *Combinational logic*


- output depends on current inputs

❑ *Sequential logic*

 - output depends on current and previous inputs
- Requires separating previous, current, future
- Called *state* or *tokens*
- Ex: FSM, pipeline




Finite State Machine

 

Pipeline


Sequencing Elements

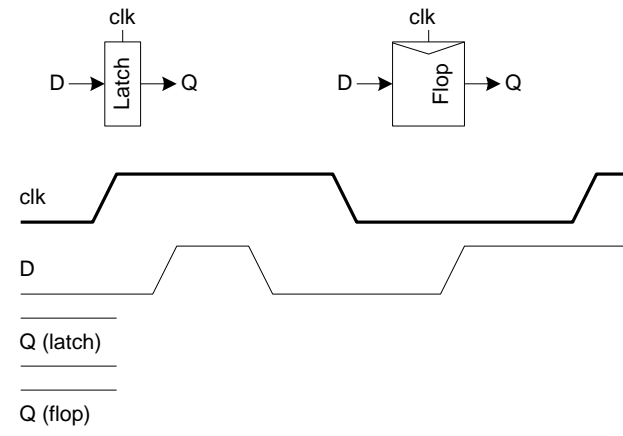- ❑ **Latch:** Level sensitive
 - a.k.a. transparent latch, D latch
- ❑ **Flip-flop:** edge triggered
 - A.k.a. master-slave flip-flop, D flip-flop, D register
- ❑ **Timing Diagrams**
 - Transparent
 - Opaque
 - Edge-trigger




Latch Design

 - ❑ Widely used in standard cells
 - + Very robust (most important)
 - Rather large
 - Rather slow (1.5 – 2 FO4 delays)
 - High clock loading



Flip-Flop Design

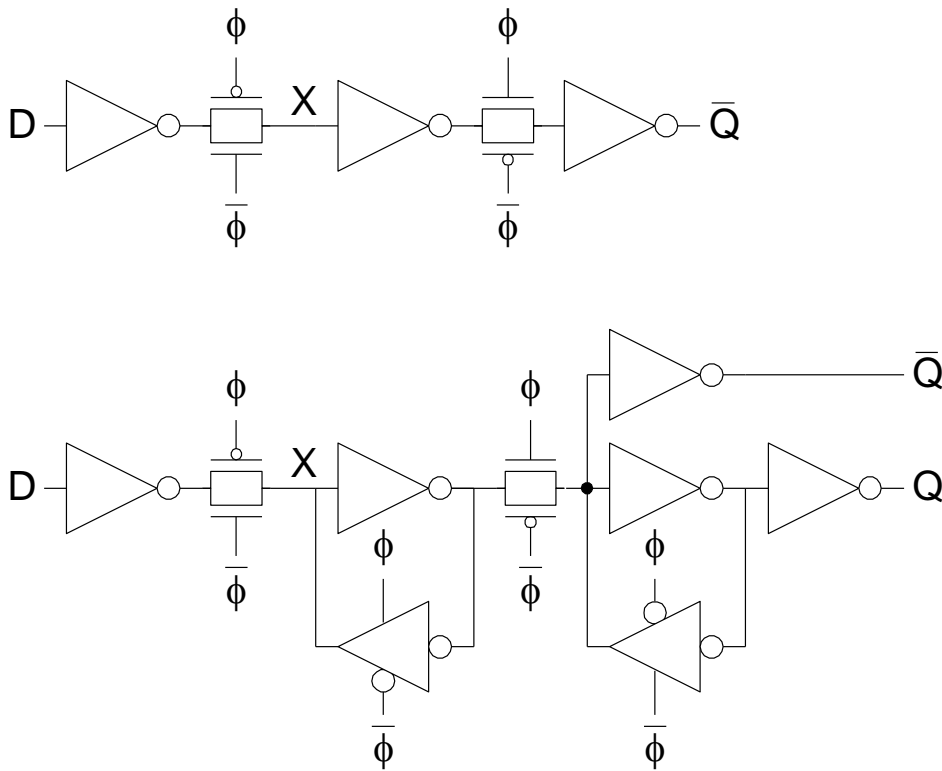
- ❑ Flip-flop is built as pair of back-to-back latches




Enable

- ❑ Enable: ignore clock when $en = 0$
 - Mux: increase latch D-Q delay
 - Clock Gating: increase en setup time, skew





Symbol

 

Multiplexer Design

 


Clock Gating Design

    


Reset

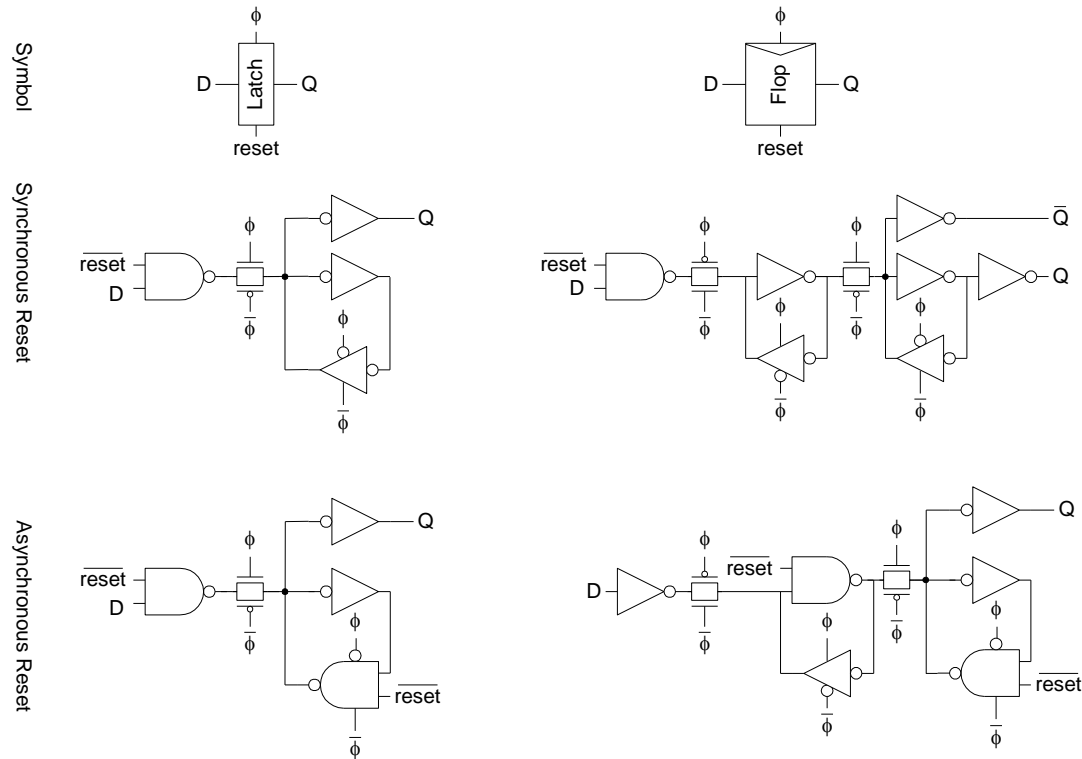- ❑ Force output low when reset asserted
- ❑ Synchronous vs. asynchronous




Set / Reset

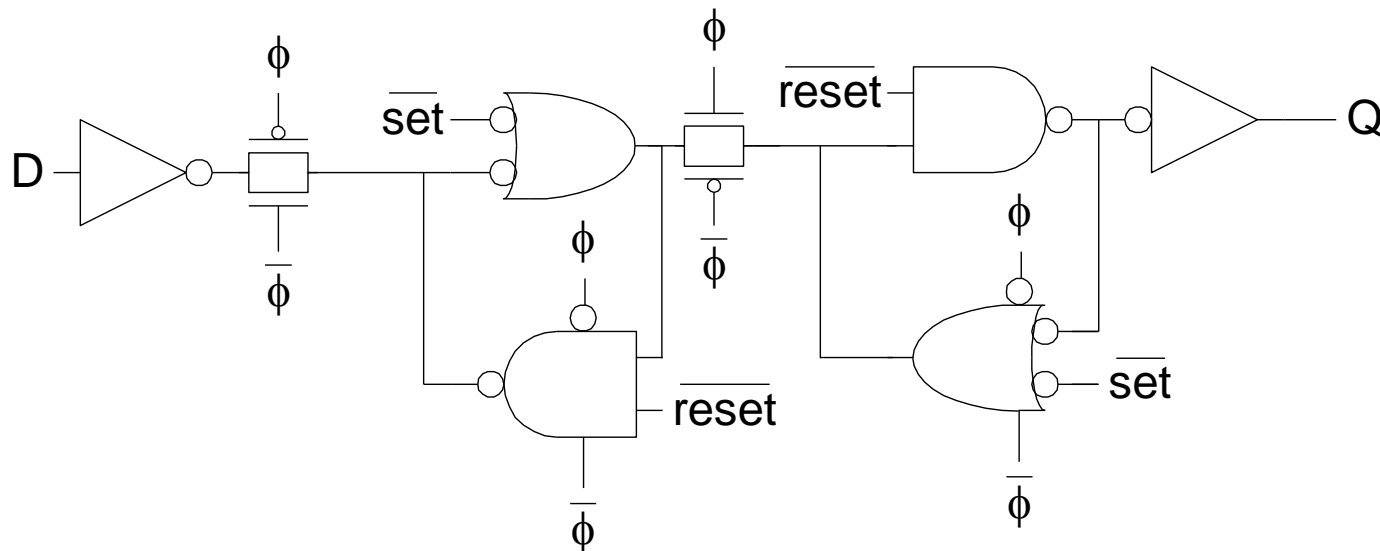- ❑ Set forces output high when enabled
- ❑ Flip-flop with asynchronous set and reset



Sequencing Methods







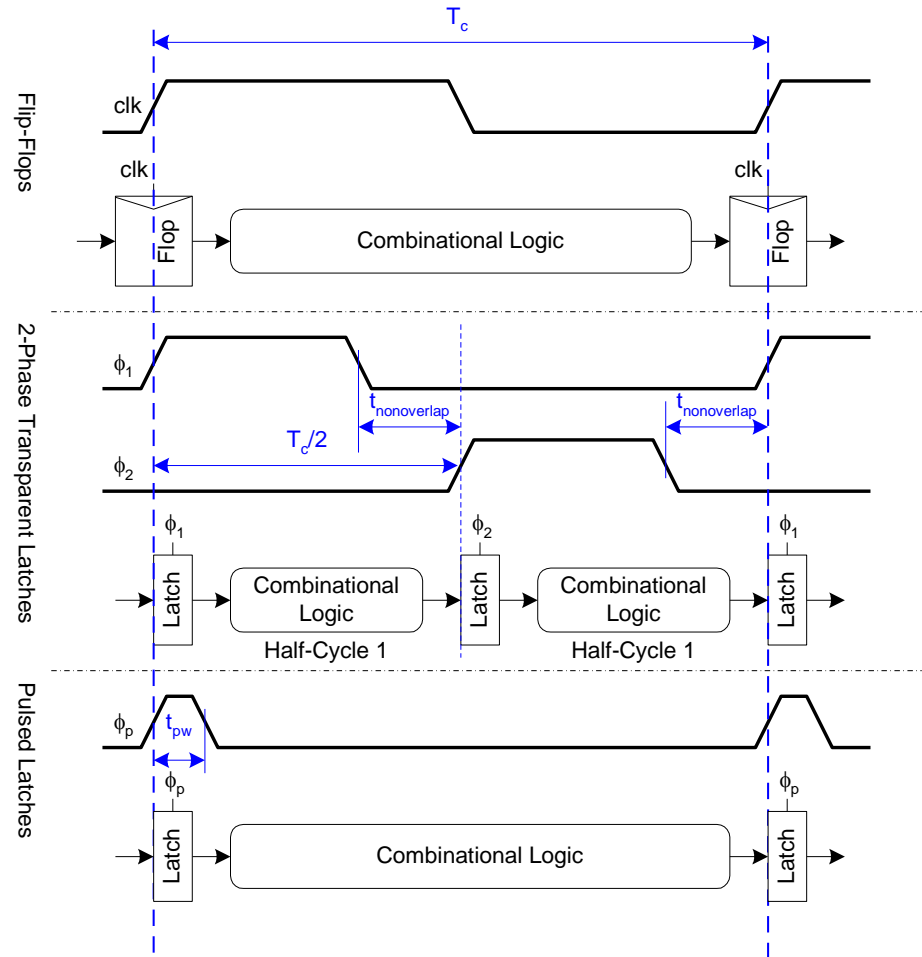
- ❑ Flip-flops
- ❑ 2-Phase Latches
- ❑ Pulsed Latches




Timing Diagrams

Contamination and Propagation Delays

t_{pd}	Logic Prop. Delay
t_{cd}	Logic Cont. Delay
t_{pcq}	Latch/Flop Clk->Q Prop. Delay
t_{ccq}	Latch/Flop Clk->Q Cont. Delay
t_{pdq}	Latch D->Q Prop. Delay
t_{cdq}	Latch D->Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time

       


Max-Delay: Flip-Flops

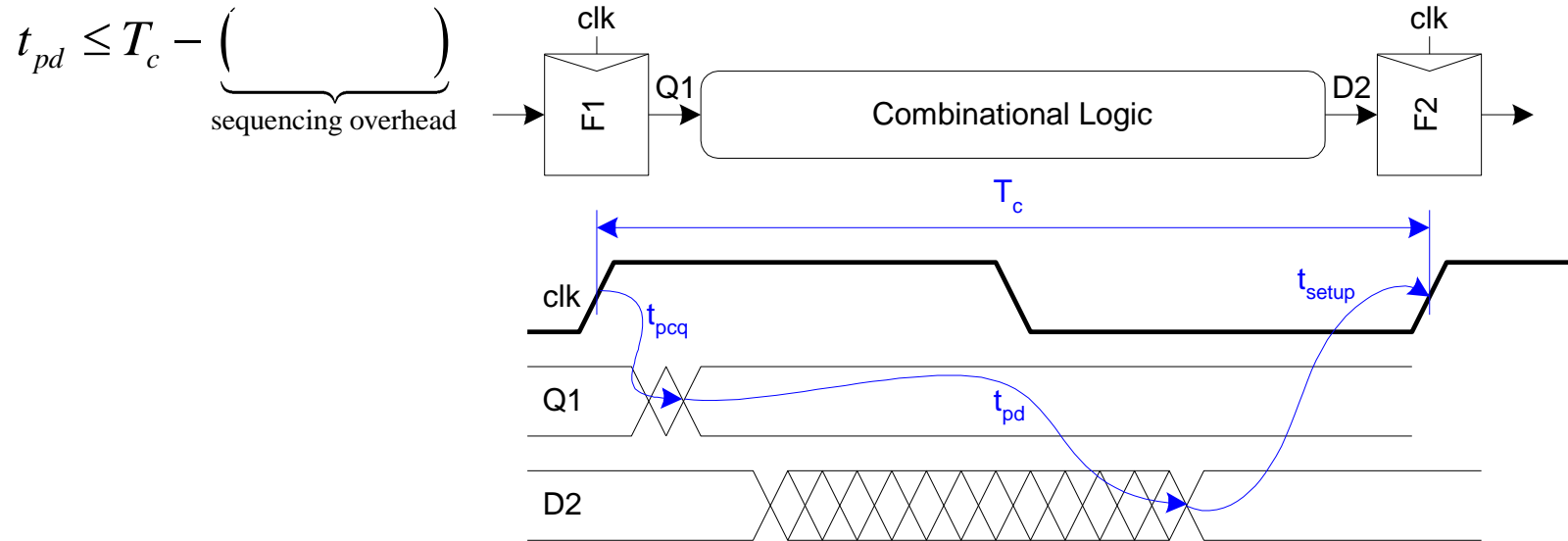


Max Delay: 2-Phase Latches
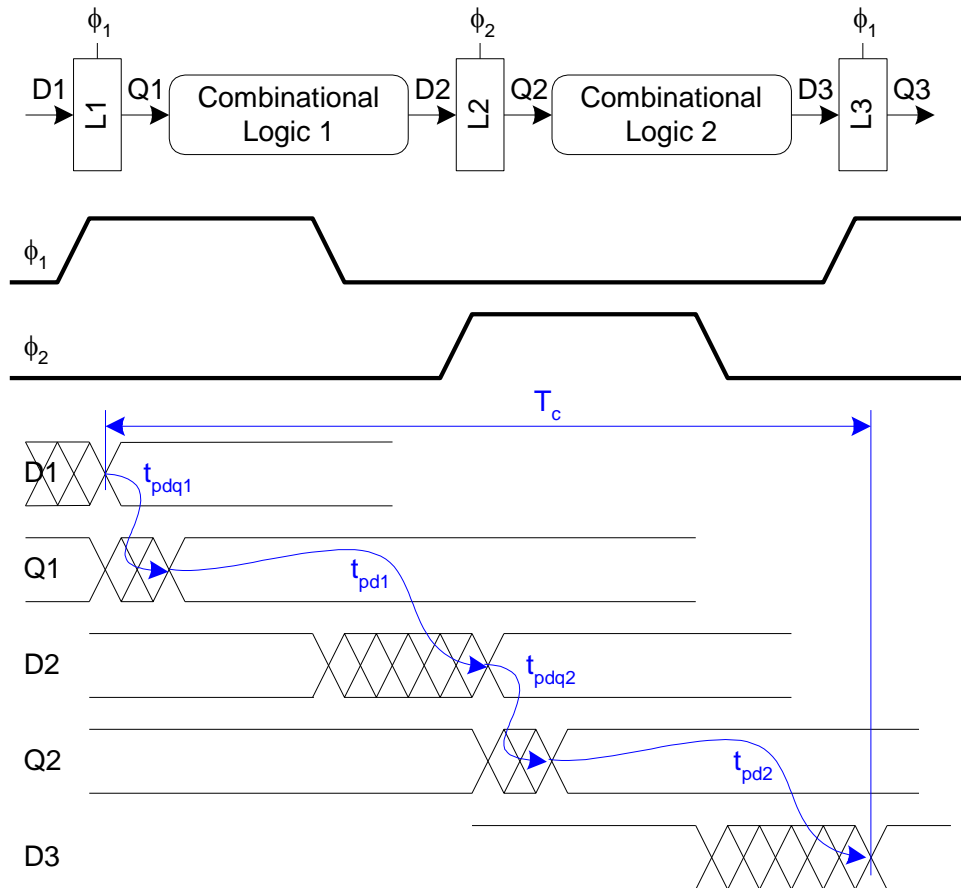
$$t_{pd} = t_{pd1} + t_{pd2} \leq T_c - \underbrace{\quad}_{\text{sequencing overhead}}$$




Max Delay: Pulsed Latches
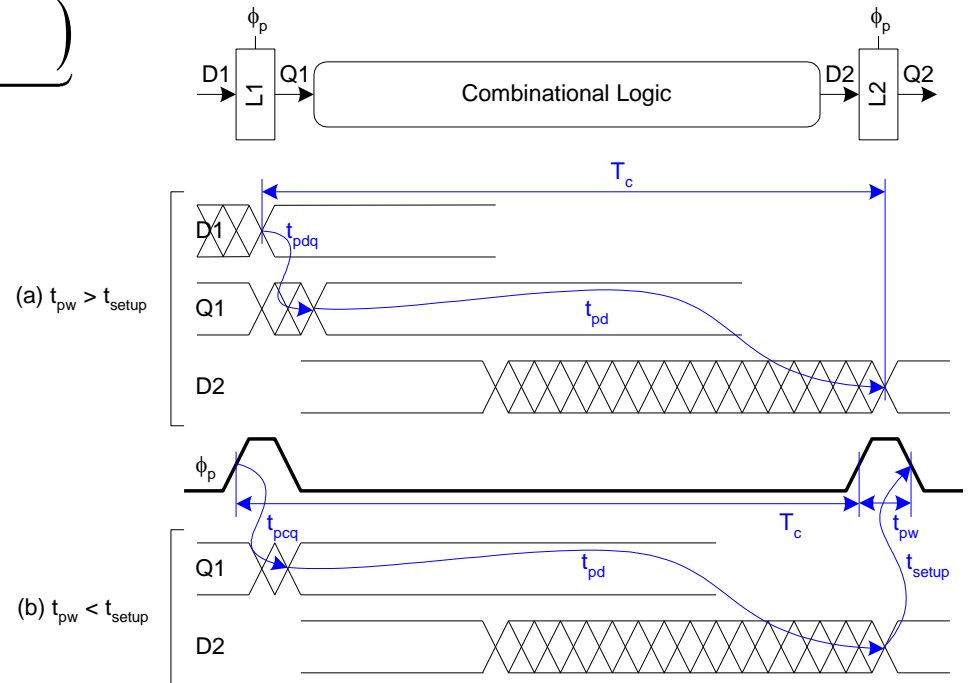
$$t_{pd} \leq T_c - \underbrace{\max(\quad)}_{\text{sequencing overhead}}$$



Min-Delay: Flip-Flops

$$t_{cd} \geq$$

 


Min-Delay: 2-Phase Latches

$$t_{cd1}, t_{cd2} \geq$$

Hold time reduced by nonoverlap

Paradox: hold applies twice each cycle, vs. only once for flops.


But a flop is made of two latches!

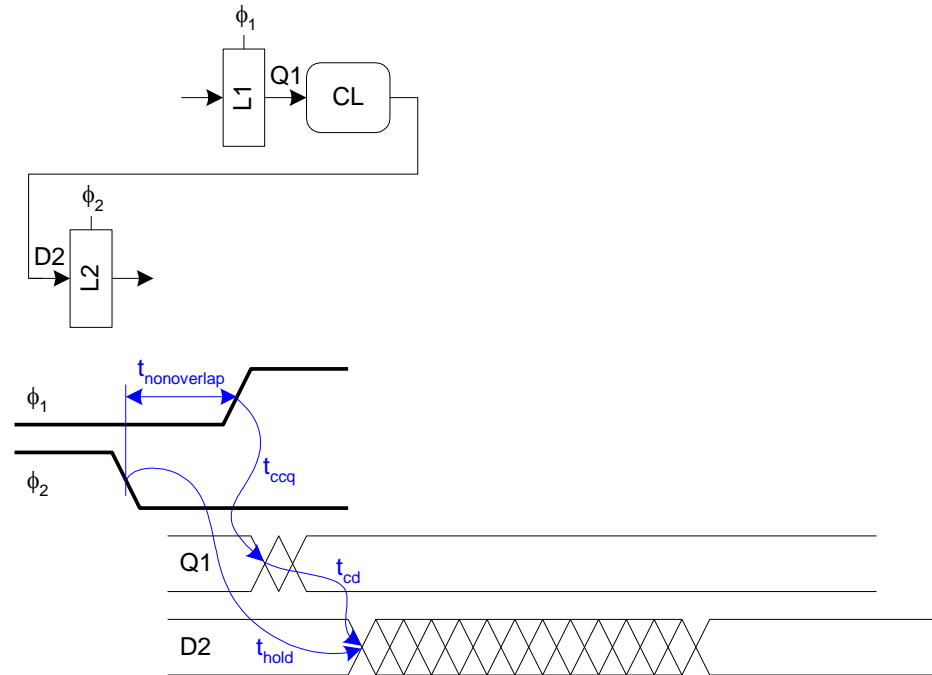

Min-Delay: Pulsed Latches

$$t_{cd} \geq$$


Hold time increased
by pulse width

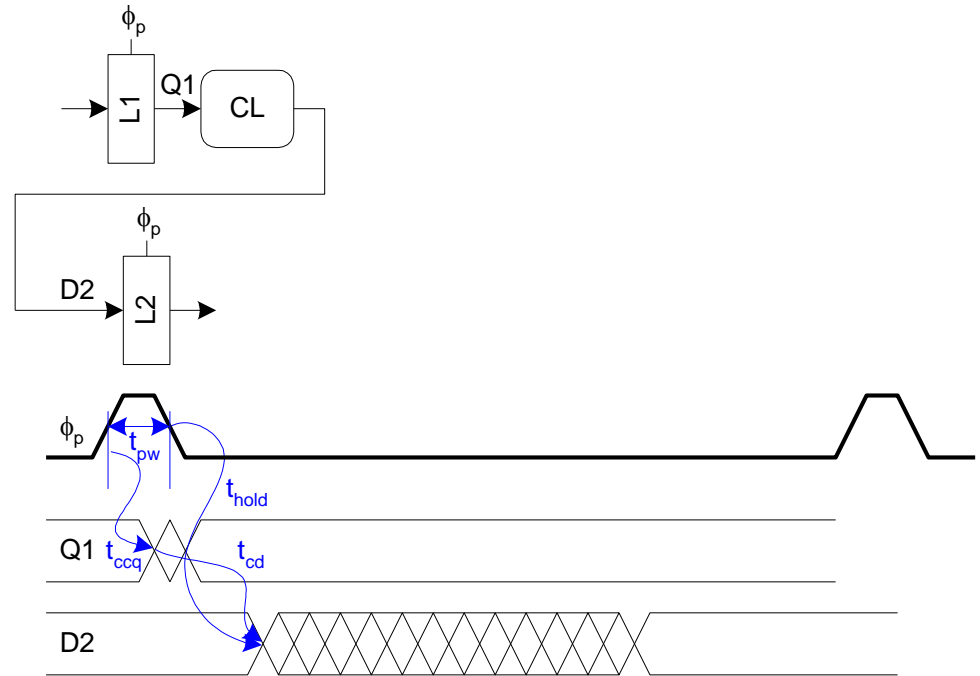

Time Borrowing

- ❑ In a flop-based system:
 - Data launches on one rising edge
 - Must setup before next rising edge
 - If it arrives late, system fails
 - If it arrives early, time is wasted
 - Flops have hard edges
- ❑ In a latch-based system
 - Data can pass through latch while transparent
 - Long cycle of logic can borrow time into next
 - As long as each loop completes in one cycle

Time Borrowing Example

 


How Much Borrowing?

2-Phase Latches

$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}})$$

Pulsed Latches

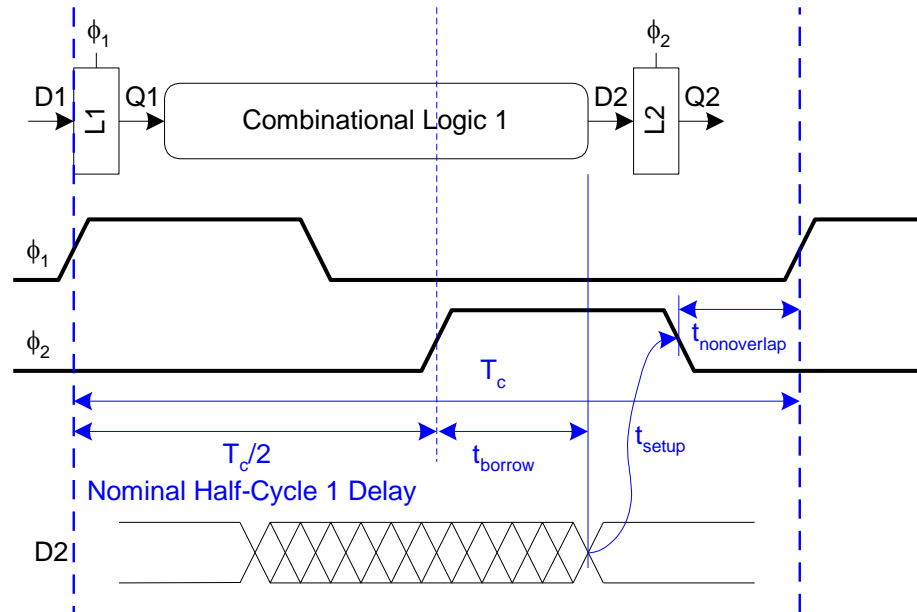
$$t_{\text{borrow}} \leq t_{pw} - t_{\text{setup}}$$



Clock Skew

- ❑ We have assumed zero clock skew
- ❑ Clocks really have uncertainty in arrival time
 - Decreases maximum propagation delay
 - Increases minimum contamination delay
 - Decreases time borrowing

Clock Uncertainties

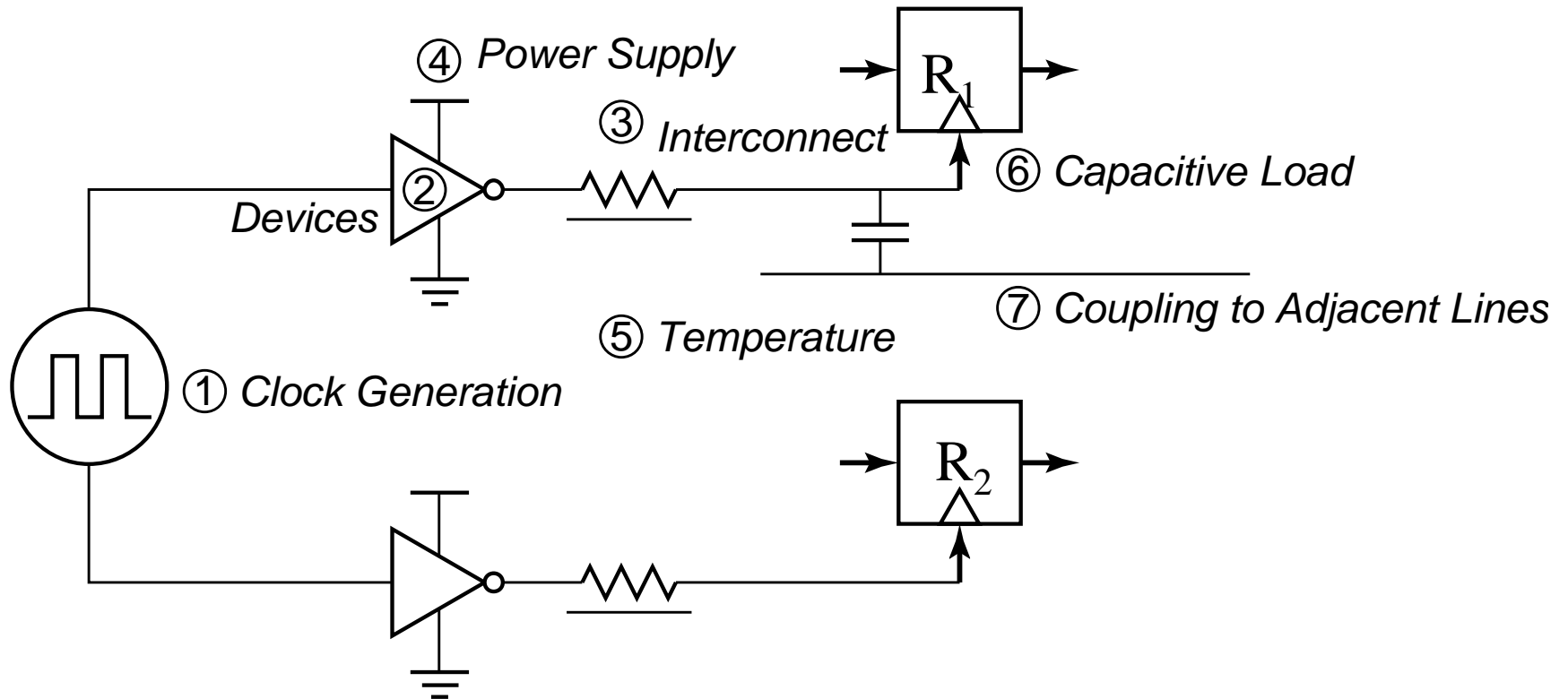

Sources of clock uncertainty

Clock Nonidealities

❑ **Clock skew**

- *Spatial variation in temporally equivalent clock edges; deterministic + random, t_{SK}*


❑ **Clock jitter**

- Temporal variations in consecutive edges of the clock signal; modulation + random noise
- Cycle-to-cycle (short-term) t_{JS}
- Long term t_{JL}

❑ **Variation of the pulse width**


- Important for level sensitive clocking [latches]

Clock Skew and Jitter

 

- ❑ Both skew and jitter affect the effective cycle time
- ❑ Only skew affects the race margin


Clock Skew

 

Skew: Flip-Flops

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
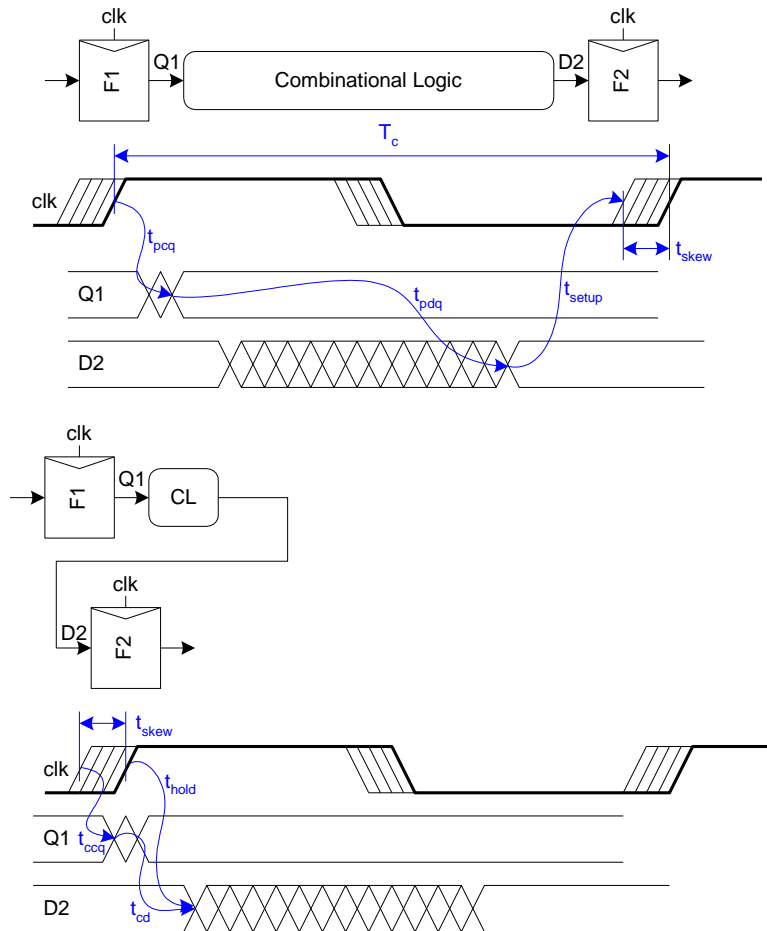
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$




Skew: Latches

2-Phase Latches

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}} + t_{\text{skew}}$$
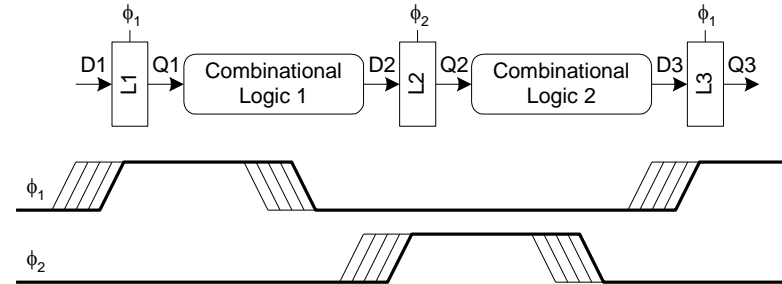
$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}} + t_{\text{skew}})$$



Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{\text{setup}} - t_{pw} + t_{\text{skew}})}_{\text{sequencing overhead}}$$

$$t_{cd} \geq t_{\text{hold}} + t_{pw} - t_{ccq} + t_{\text{skew}}$$


$$t_{\text{borrow}} \leq t_{pw} - (t_{\text{setup}} + t_{\text{skew}})$$

Two-Phase Clocking

- ❑ If setup times are violated, reduce clock speed
- ❑ If hold times are violated, chip fails at any speed
- ❑ No tools to analyze clock skew
 - An easy way to guarantee hold times is to use 2-phase latches with big nonoverlap times
- ❑ Call these clocks ϕ_1 , ϕ_2 (ph1, ph2)

Safe Flip-Flop

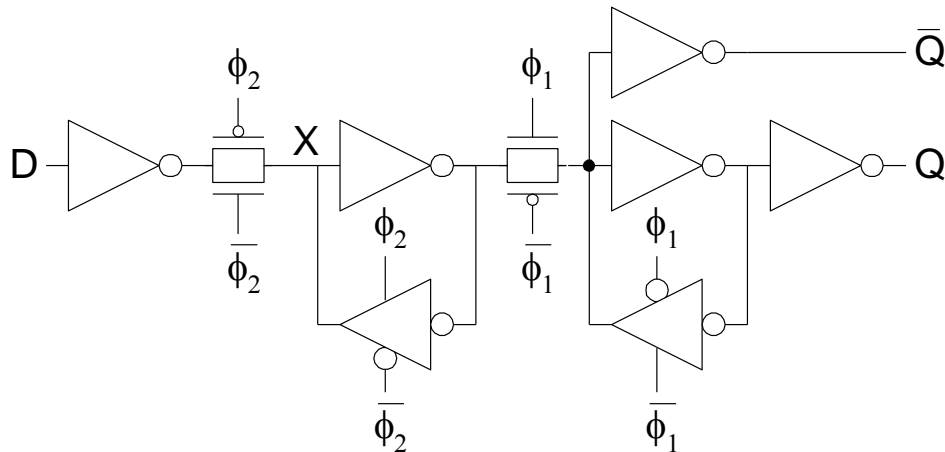- ❑ Past years used flip-flop with nonoverlapping clocks
 - Slow – nonoverlap adds to setup time
 - But no hold times
- ❑ In industry, use a better timing analyzer
 - Add buffers to slow signals if hold time is at risk



Sequencing Summary

- ❑ Flip-Flops:
 - Very easy to use, supported by all tools
- ❑ 2-Phase Transparent Latches:
 - Lots of skew tolerance and time borrowing
- ❑ Pulsed Latches:
 - Fast, some skew tol & borrow, hold time risk

	Sequencing overhead ($T_c - t_{pd}$)	Minimum logic delay t_{cd}	Time borrowing t_{borrow}
Flip-Flops	$t_{pcq} + t_{setup} + t_{skew}$	$t_{hold} - t_{ccq} + t_{skew}$	0
Two-Phase Transparent Latches	$2t_{pdq}$	$t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$ in each half-cycle	$\frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$
Pulsed Latches	$\max(t_{pdq}, t_{pcq} + t_{setup} - t_{p\omega} + t_{skew})$	$t_{hold} - t_{ccq} + t_{p\omega} + t_{skew}$	$t_{p\omega} - (t_{setup} + t_{skew})$

Reference

- ❑ Reference [1]. Chapter 10.1-10.3

STA in ASIC Design Flow

